

Shri Ramdeobaba College of Engineering and Management, Nagpur-13.
Department of Electronics Engineering
Analog and Digital Communication Engineering Lab [ENP357]
Even Semester – 2023-24

Lab 01

Amplitude Modulation

Name:	Pawan Dilip Sorte
Batch / Roll No:	A1/12
Semester/Section:	6 th / A
Date of Performance:	16/1/2024
Date of Submission:	17/4/2024
Name & Signature of Faculty:	Mrs.Rohini Ochawar


Lab-01

- Aim:** Design, Simulate and Implementation of transistor based AM Modulator and plotting AM signals for modulation indices $m = 1$, $m < 1$ and $m > 1$

✓ **Apparatus:** CRO,DSO,Transistor BC107,Resistors,inductor,capacitor

✓ **Software Used:** Multisim

✓ **Circuit Diagram:**

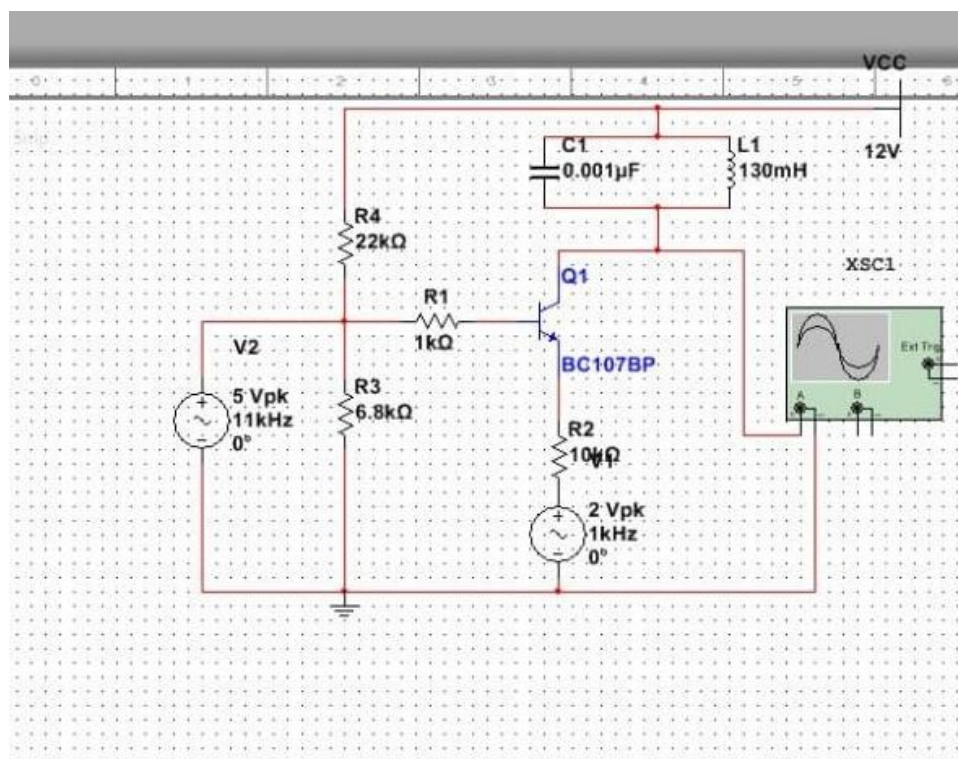

✓ **Observation Table**

Table No. 1: Calculation of m based on simulation results

Frequency of Modulating signal (Hz): **Frequency of Carrier signal (Hz):**

Case	Modulating Signal Voltage (Vm)	Carrier Signal Voltage (Vc)	Modulation Index (m)
m<1	2V	5V	0.4
m>1			
m=1	5V	5V	1

Table No. 2: Calculation of m based on circuit implementation on bread board

Frequency of Modulating signal (Hz): Frequency of Carrier signal (Hz):

Case	Modulating Signal Voltage (Vm)	Carrier Signal Voltage (Vc)	Modulation Index (m)
m<1	4.096	4.75	0.857
m>1	10	5	2
m=1	5.445	6.019	0.98

✓ Calculations:

Modulation index ,

$$m = V_m / V_c$$

$$m = \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}}$$

1. $m < 1$

$$V_{\max} = 4.423 \text{ V}$$

$$V_{\min} = 0.3276 \text{ V}$$

$$m = \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}}$$

$$= \frac{4.423 - 0.3279}{4.423 + 0.3276}$$

$$= 0.857 \text{ V}$$

2. $m = 1$

$$V_{\max} = 5.732 \text{ V}$$

$$V_{\min} = 0.287 \text{ V}$$

$$m = \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}}$$


$$= \frac{5.732 - 0.287}{5.732 + 0.287}$$



$$= 0.98 \text{ V}$$

$1.m > 1$
 $V_c = 5V_{pp}$
 $V_m = 10V_{pp}$
 $m = 10/5$
 $= 2$



✓ Obtained Waveforms/Simulation Results:

Part 1:

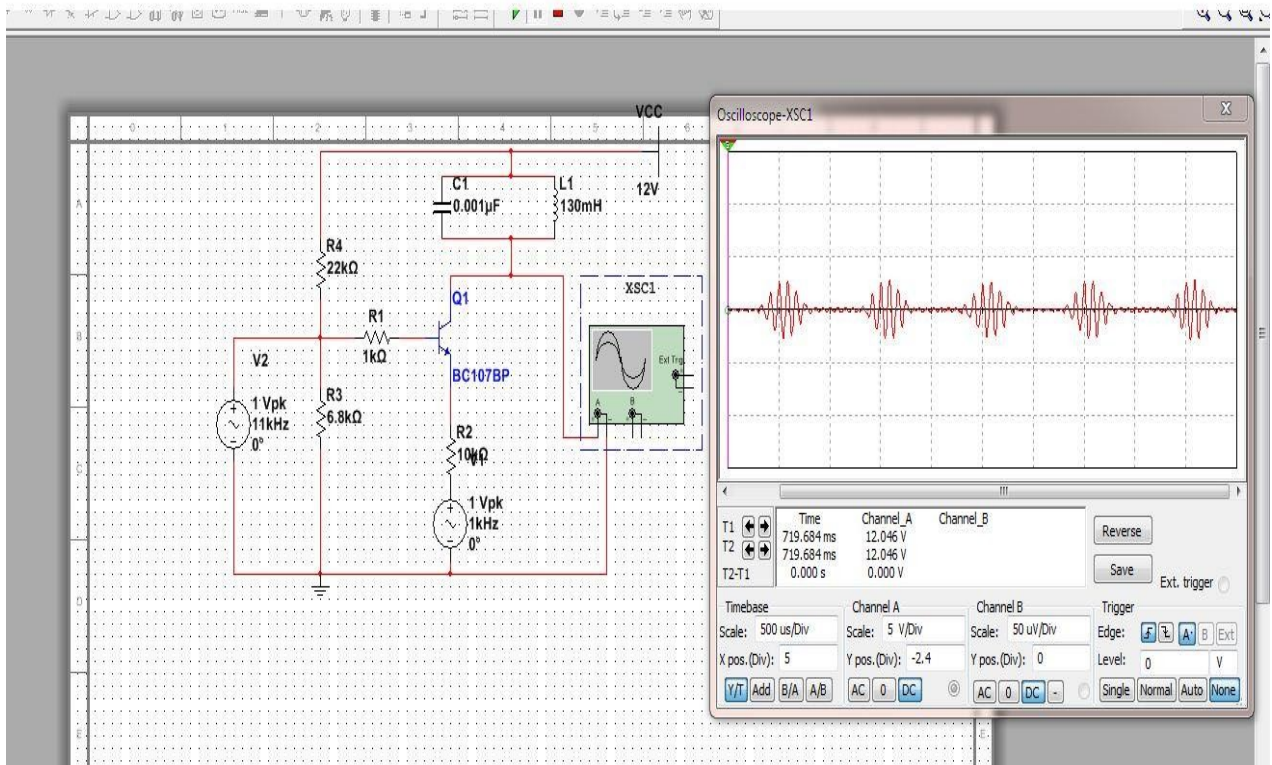

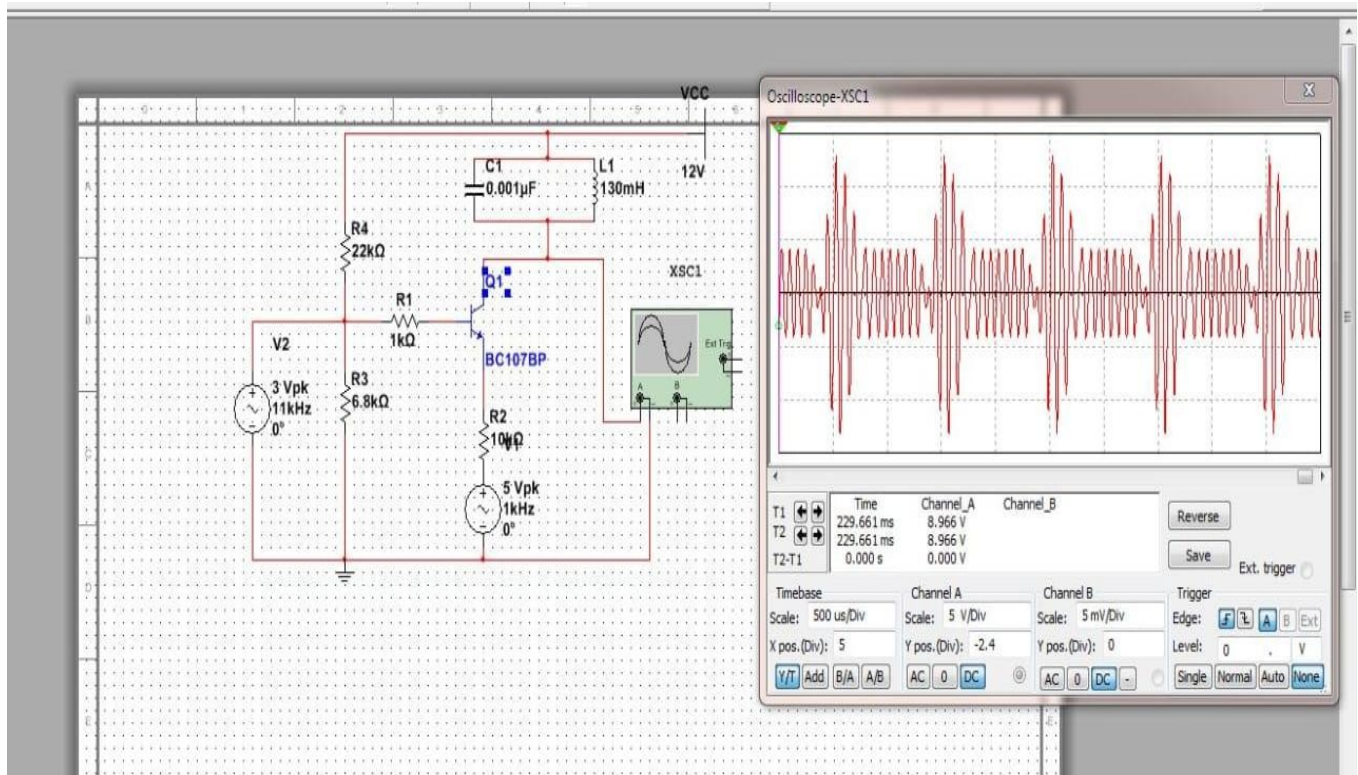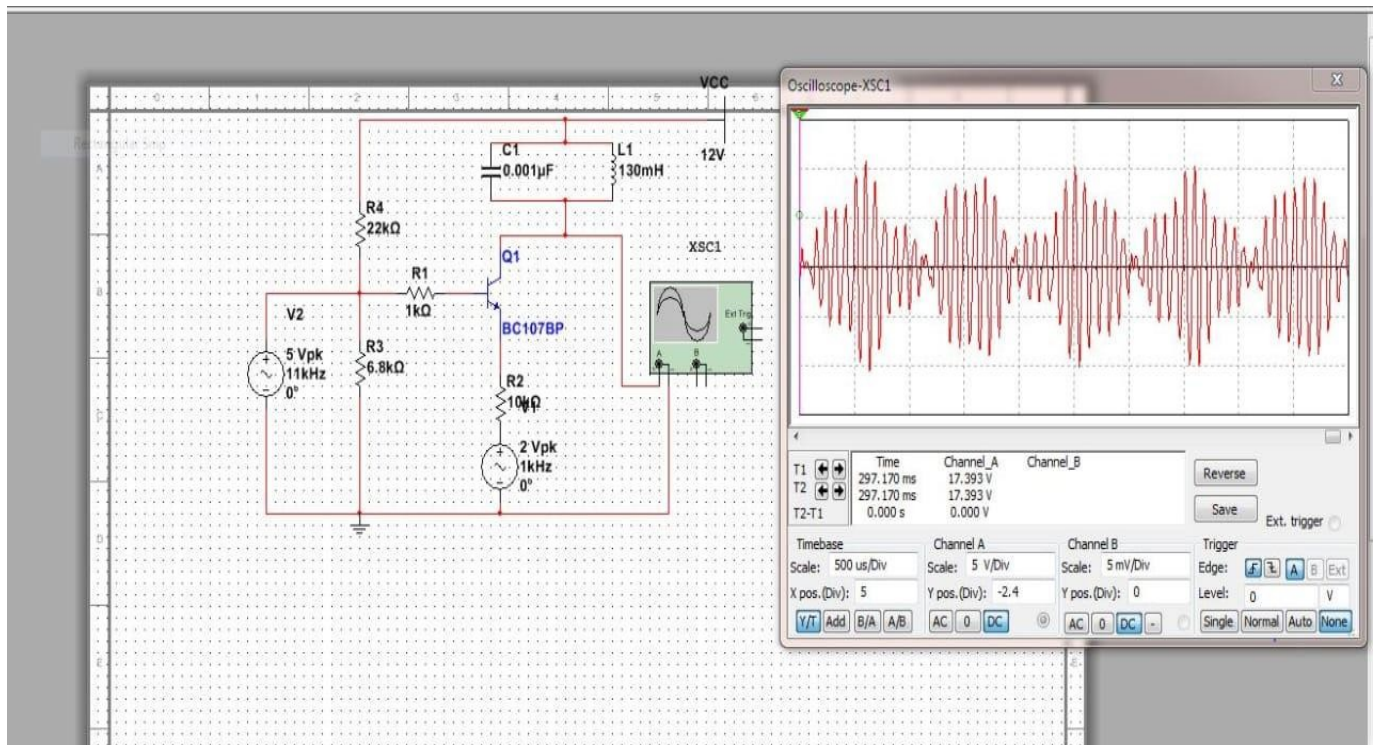

Part 2:

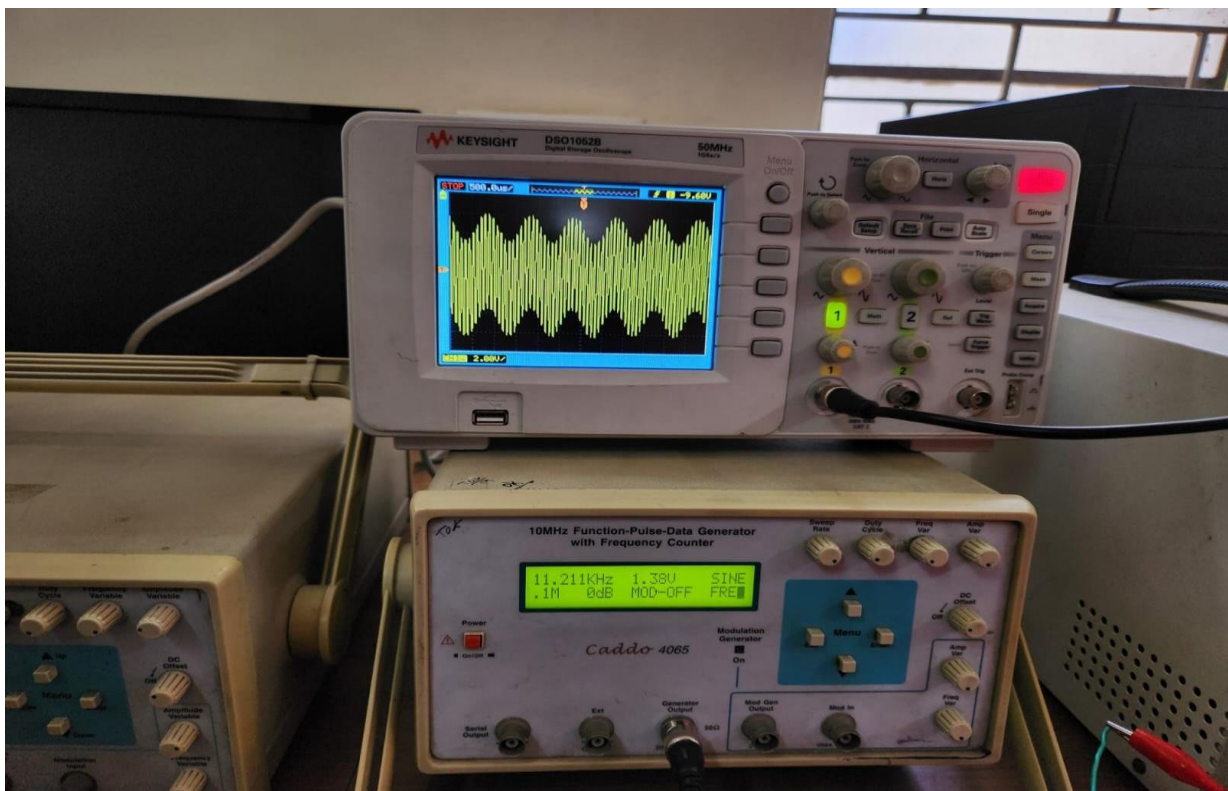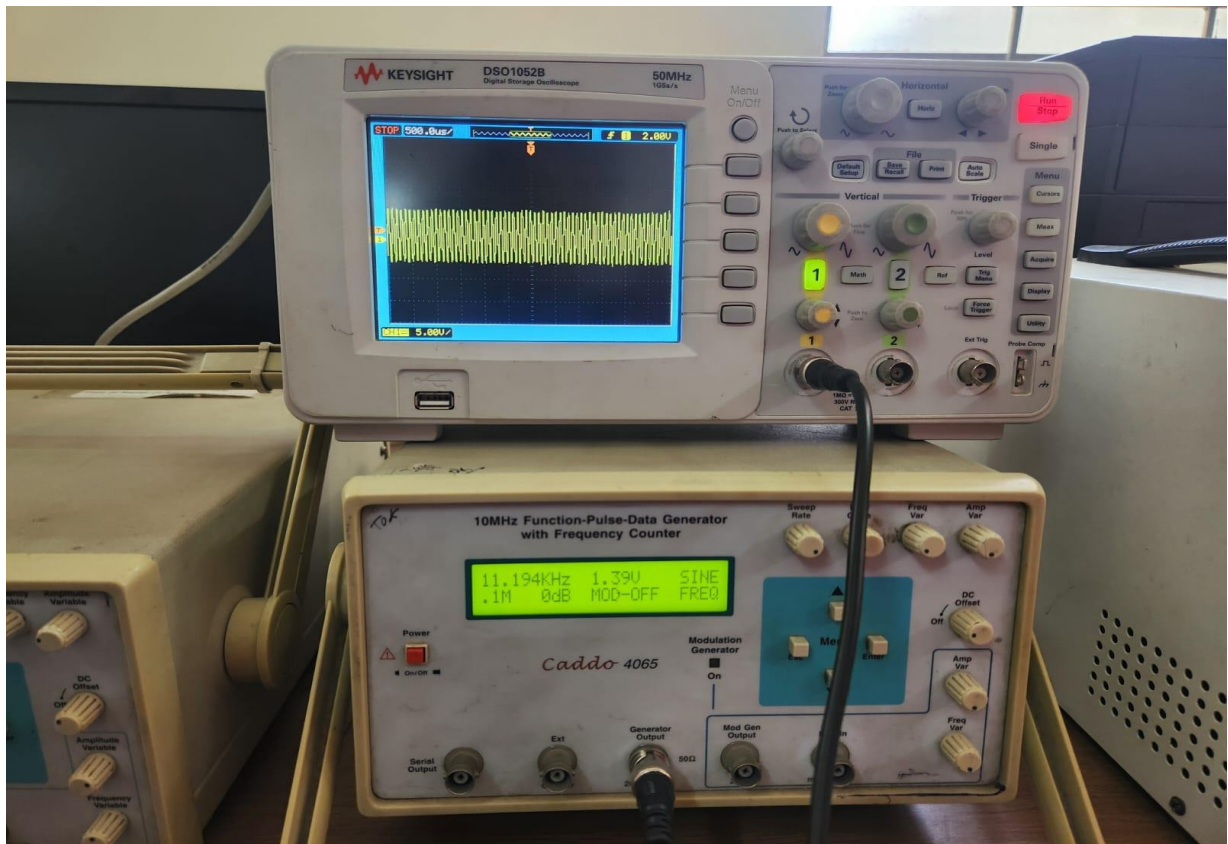

✓ Discussion and Conclusion:

The waveform for modulation index $m > 1$, $m = 1$, $m < 1$ was observed according to Modulation index the change in the waveform was observed. It is observed that an amplitude of modulating signal increases, the amplitude of envelope also increases and as amplitude message signal decreases, the amplitude of AM envelope also decreases. It is observed that the frequency of envelope is equal to frequency of modulating Signal.