

Shri Ramdeobaba College of Engineering and Management, Nagpur-13.
Department of Electronics Engineering
Analog and Digital Communication Engineering Lab [ENP357]
Even Semester – 2023-24

Lab 06

Amplitude Shift Keying

Name:	Pawan Dilip Sorte
Batch / Roll No. :	A1/12
Semester/Section:	6 th /A
Date of Performance:	20/3/2023
Date of Submission:	17/4/2024
Name & Signature of Faculty :	<u>Mrs. Rohini Ochawar</u>


Lab-06

Aim: Design and simulation of transistor based ASK modulator.


✓ **Software Used:** MULTISIM

✓ **Circuit Diagram:**


CARRIER SIGNAL:

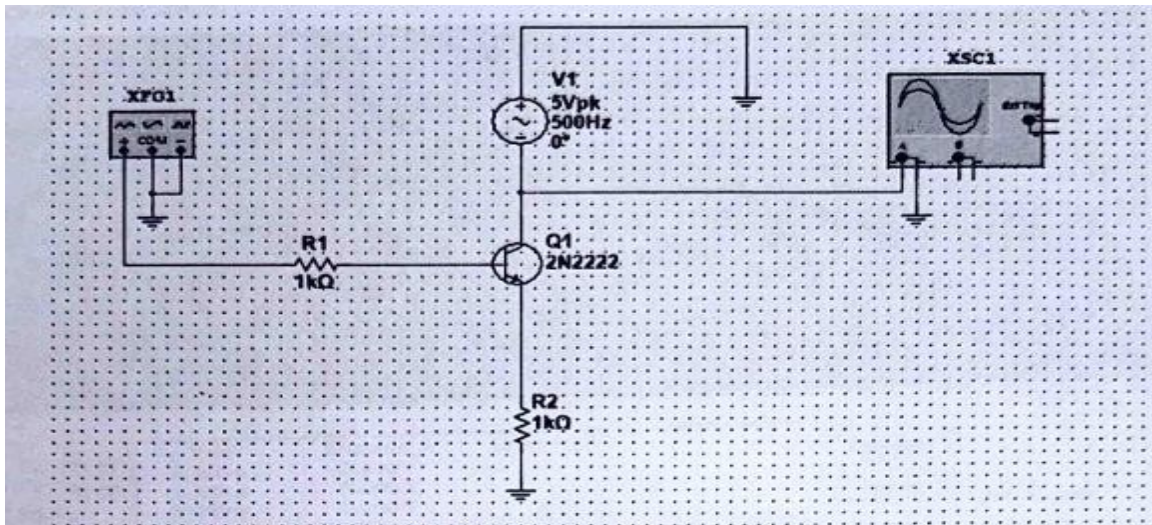

MODULATOR ASK:

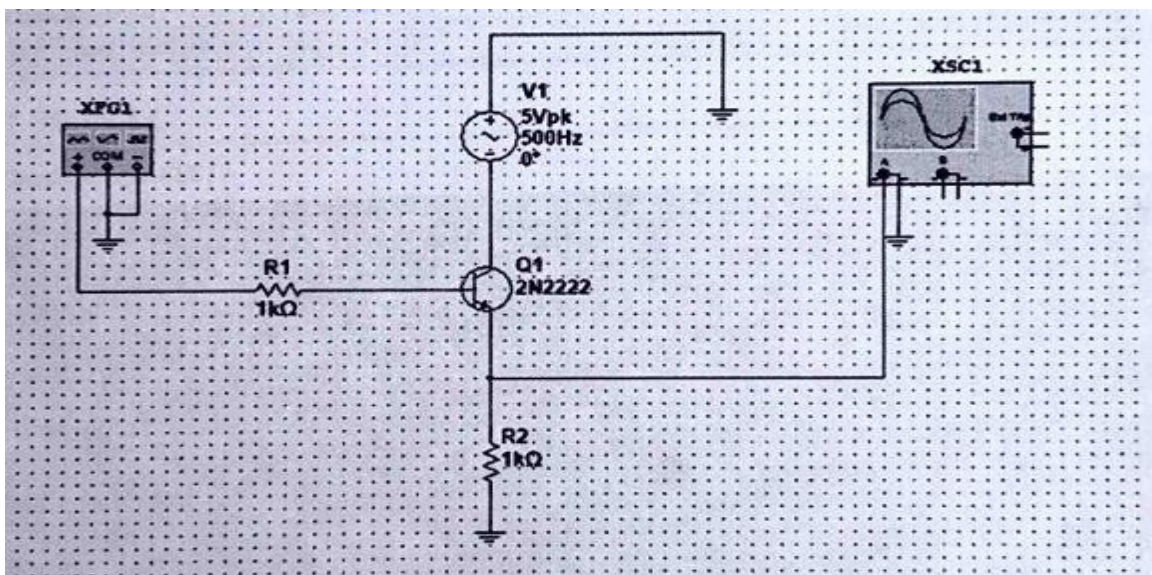

DEMODULATOR ASK:

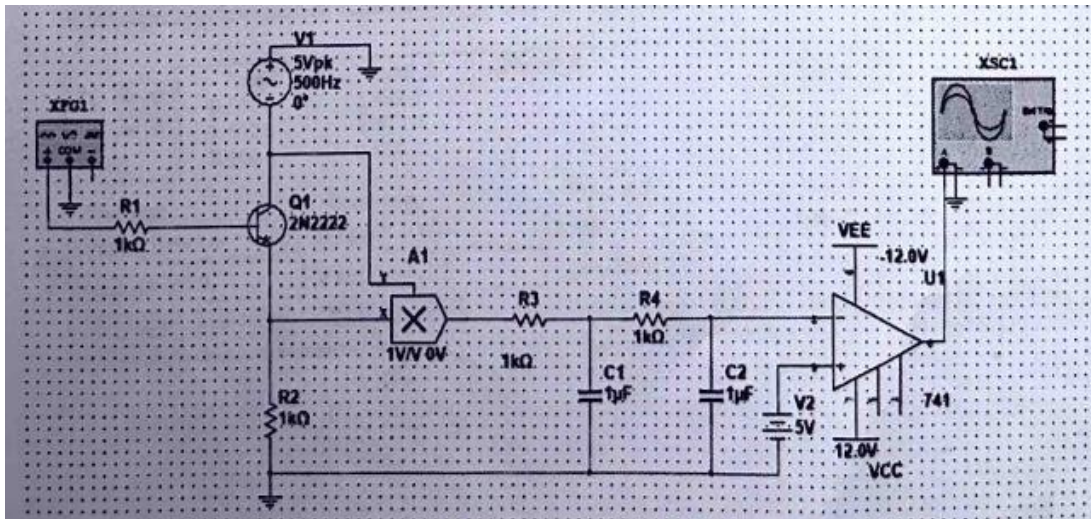

✓ Observations

Modulating signal voltage: 5V , frequency : 100 HZ.


Carrier signal voltage : 5V , frequency: 500 HZ.

Observed waveform ASK:


ASK OUTPUT:




DATA:

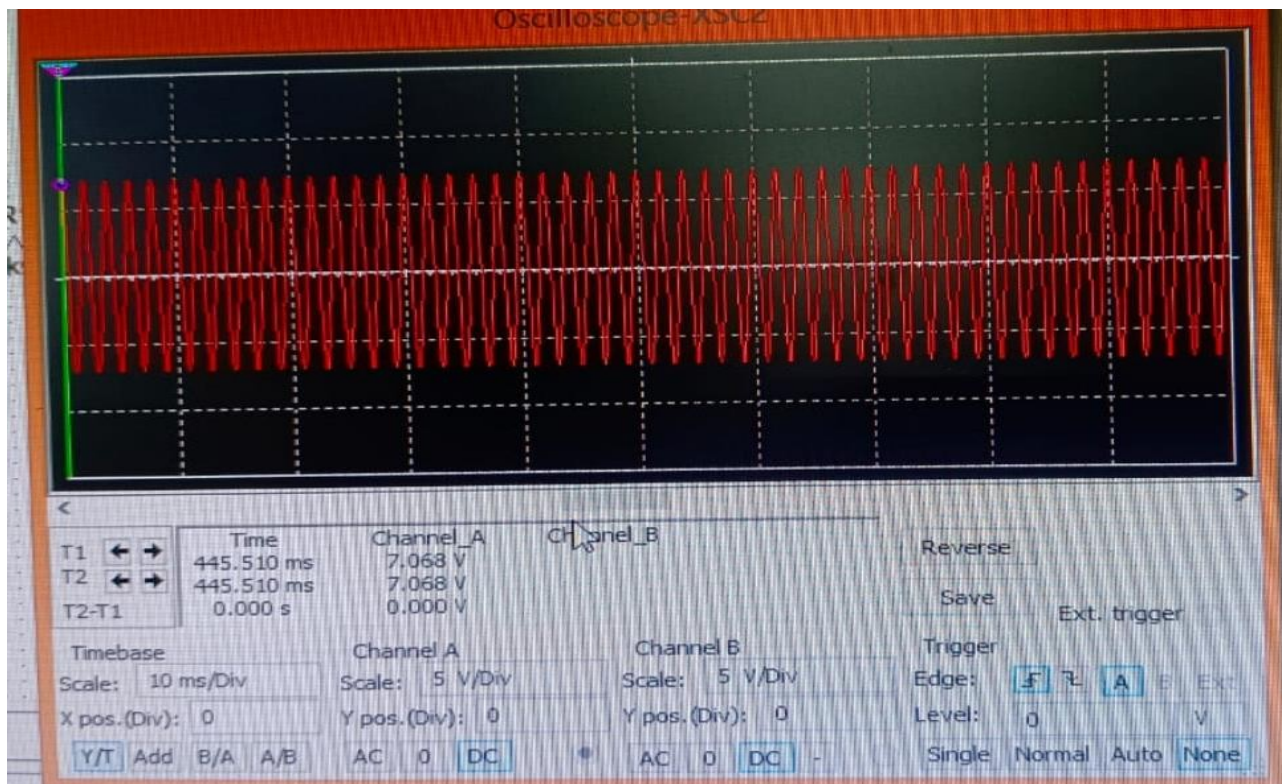

CARRIER:

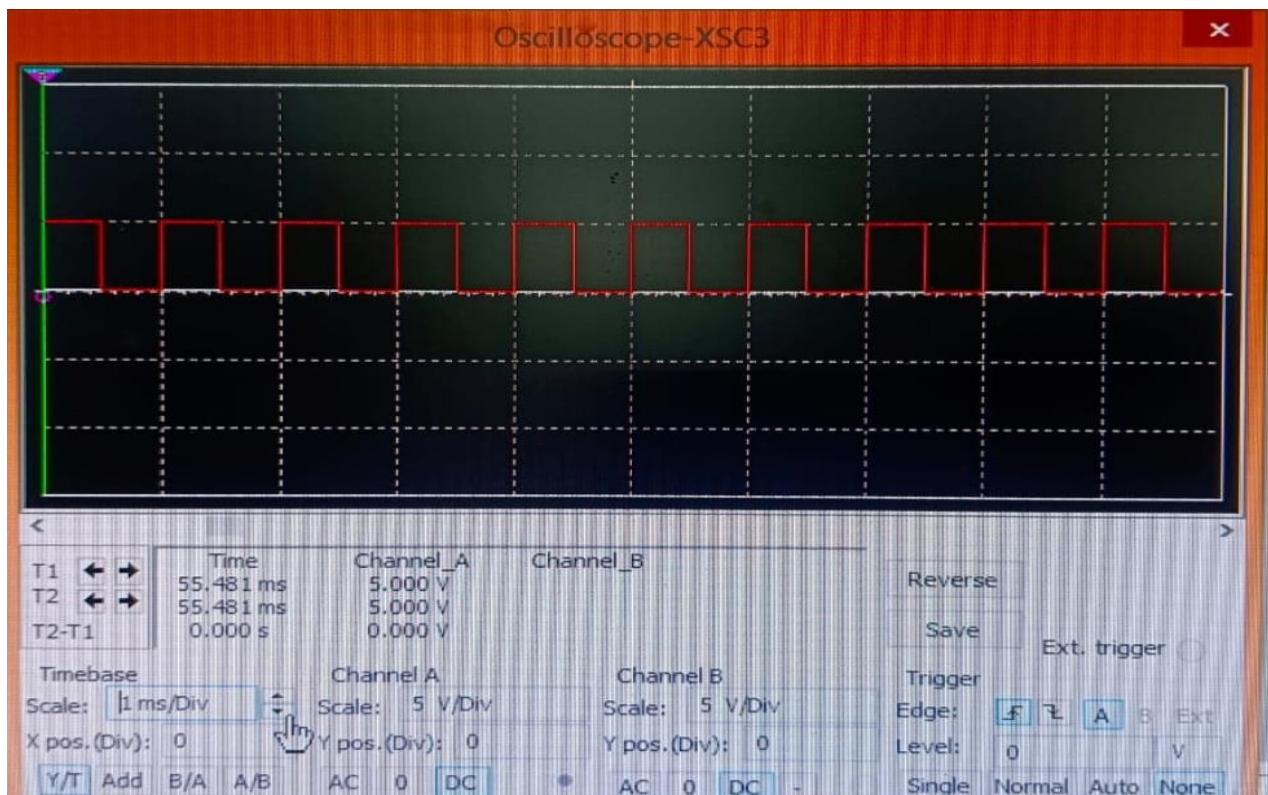

DEMODULATOR:

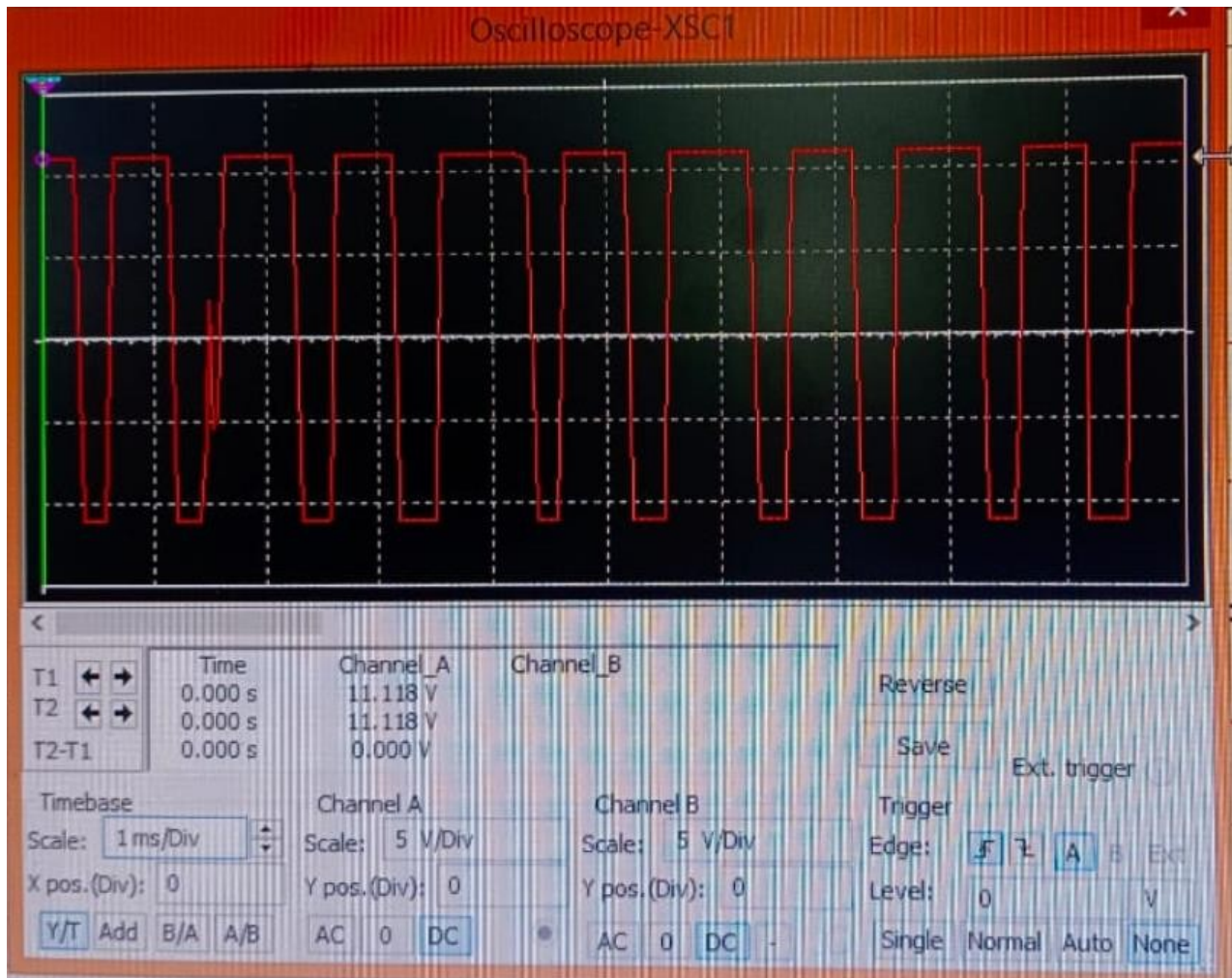

Conclusion:

The transistor-based ASK modulator can be an effective way to transmit data over a communication channel using amplitude modulation.